

ELECENG 2CJ4

## Lab 5 Report

Butterworth Low-Pass Filter

4/02/2025

Jasmine Dosanjh – L03 – dosanj5 – 400531879

Akinniyi Chidiebube – L03 – akinniy - 400501611

## 1. Introduction

Active filters are widely used in analog circuits, i.e. in power, communication, and control systems. In this experiment, we will study the second-order Butterworth Salleny-key low-pass filter.

## 2. Operational Principle of the experiment

a) Deriving an expression for the transfer function of the filter using the Sallen-Key Transfer Function with  $R_4 = 0$ ,  $R_3 = \infty$  ( $K = 1$ )

$$H(s) = \frac{1}{R_1 R_2 C_1 C_2 s^2 + s(R_1 C_1 + R_2 C_1) + 1}$$

Where  $R_1 = R_2$ ,  $C_1 = C_2$

Therefore,

$$H(s) = \frac{1}{R^2 C^2 s^2 + 2sRC + 1}$$

Let  $s = j\omega = j(2\pi f)$

$$H(j \cdot 2\pi f) = \frac{1}{R^2 C^2 (j \cdot 2\pi f)^2 + 2(j \cdot 2\pi f)RC + 1}$$

$$H(j \cdot 2\pi f) = \frac{1}{[1 - (2RC\pi f)^2] + j(4\pi fRC)}$$

$$|H(j \cdot 2\pi f)| = \frac{1}{\sqrt{[1 - (2RC\pi f)^2]^2 + [4\pi fRC]^2}}$$

b) The cut-off frequency of the filter is


$$f_c = \frac{1}{2\pi RC} = \frac{1}{2\pi(10k\Omega)(100nF)} = 159.15 \text{ Hz}$$

c) Evaluating the filter transfer function for the varying frequencies can be seen in the Table below.

Table 1. Theoretical Gain for Varying Frequencies

Frequency	Gain $\left  \frac{V_o}{V_i} \right $ (analytical)
50 Hz	0.91017
100 Hz	0.71695
200 Hz	0.3877
500 Hz	0.092
1 kHz	0.0247
1.1 kHz	0.0205
1.2 kHz	0.0173
1.3 kHz	0.0147
1.4 kHz	0.0128
1.5 kHz	0.0111
1.6 kHz	0.0098
1.7 kHz	0.0087
1.8 kHz	0.0078
1.9 kHz	0.0070
2 kHz	0.0063
5 kHz	0.0010

The resulting waveform is shown below:

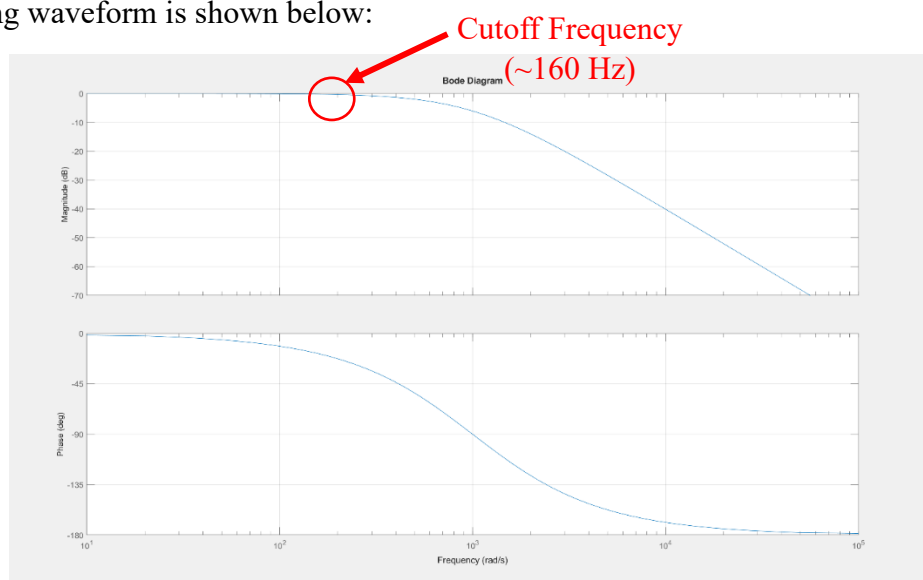

### 3. Measurement results

The AD3 measurement results are included in the table below.

Table 1. Measured Gain for Varying Frequencies

Frequency	Gain $\left  \frac{V_o}{V_i} \right $ (measured)
50 Hz	0.9103
100 Hz	0.72546
200 Hz	0.403125
500 Hz	0.098871
1 kHz	0.027475
1.1 kHz	0.0248446
1.2 kHz	0.019552
1.3 kHz	0.016714
1.4 kHz	0.014499
1.5 kHz	0.012661
1.6 kHz	0.011122
1.7 kHz	0.009964
1.8 kHz	0.008905
1.9 kHz	0.008006
2 kHz	0.007211
5 kHz	0.001385

Sample Measurement:

For  $f = 50\text{Hz}$ :

$$\text{Gain} = \frac{|V_o(\text{amplitude})|}{|V_i(\text{amplitude})|} = \frac{1.8149 \text{ V}}{1.9938 \text{ V}} = 0.9103$$

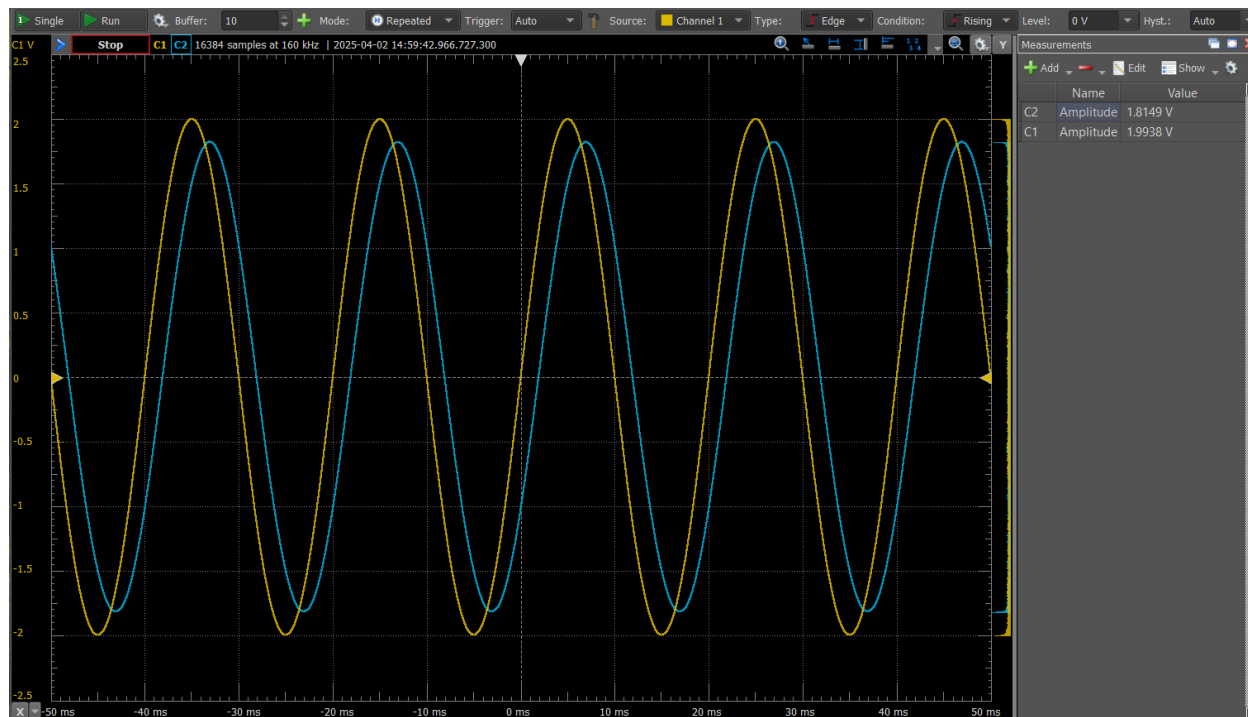


Figure 1. Resulting waveform for 50 Hz

## 4. Discussion

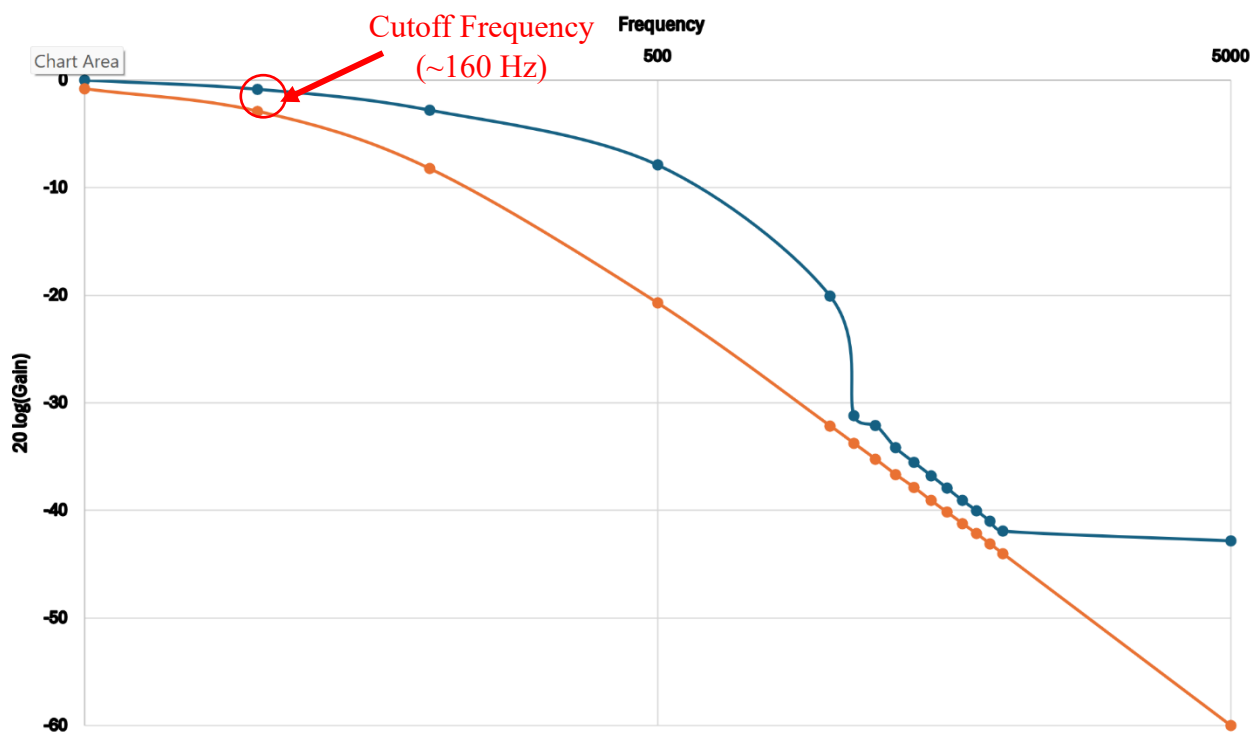


Figure 2 Graph of Measured Decibel Values against Frequency (On a logarithmic scale)

The theoretical vs measured results are very similar. This can be seen from the two graphs in the provided document. They both show that the cutoff is approx. 159.15 Hz but there is some error due to component tolerances.