

ELECENG 2CJ4

Lab 4 Report

Analyzing First-order Circuits

3/19/2025

Jasmine Dosanjh – L03 – dosanj5 – 400531879

Akinniyi Chidiebube – L03 – akinniy - 400501611

1. Introduction

2. Operational Principle of the experiment

We must determine the period and frequency voltage of the oscillator in Figure 9.

$$T = T_1 + T_2 = R_3 C \left[\ln \left(\frac{V_{sat}^+ - V_{th2}}{V_{sat}^+ - V_{th1}} \right) + \ln \left(\frac{V_{sat}^- - V_{th1}}{V_{sat}^- - V_{th2}} \right) \right] \rightarrow (17)$$

$$V_{th1} = \frac{R_2}{R_1 - R_2} V_{sat}^+ = \frac{1k\Omega}{22k\Omega - 1k\Omega} \times 5V \approx 0.238V$$

$$V_{th1} = \frac{R_2}{R_1 - R_2} V_{sat}^- \approx -0.238V$$

Plugging in the required values into Eq.17:

$$T = 1k\Omega \times 100nF \left[\ln \left(\frac{5 + 0.238}{5 - 0.238} \right) + \ln \left(\frac{-5 - 0.238}{-5 + 0.238} \right) \right]$$

****use 1k or 22k??**

Use 50k.

$$T \approx 0.95\mu S \text{ **check with TA}$$

Thus, the frequency can be found by:

$$f = \frac{1}{T}$$

3. Measurement results

The AD3 measurement results and their resulting waveforms and circuits are included below.

4. Discussion

Comparing Theoretical vs Measured Results:

$$\text{percent difference} = \frac{|C - M|}{\left(\frac{C + M}{2}\right)} \times 100$$

Generating a Triangular Output: